

1 Objective

The objective of this experiment is to demonstrate the application of simple Boolean operations using a Programmable Logic Controller (PLC). The experiment involves implementing a ladder logic diagram to control an output based on the AND and OR Boolean operations, utilizing specific input switch combinations.

2 Equipment

The following equipment is required for this experiment:

1. Siemens S7 1200 PLC Module or LOGO PLC.
2. PC with TIA PORTAL or LOGO SOFT Comfort installed.

3 Lab Work

In this section, the provided ladder diagram is developed using the appropriate software (TIA PORTAL for Siemens S7 1200 or LOGO SOFT Comfort for LOGO PLC). After creating the ladder logic, it is uploaded to the PLC module and executed to verify the functionality.

3.1 Ladder Diagram

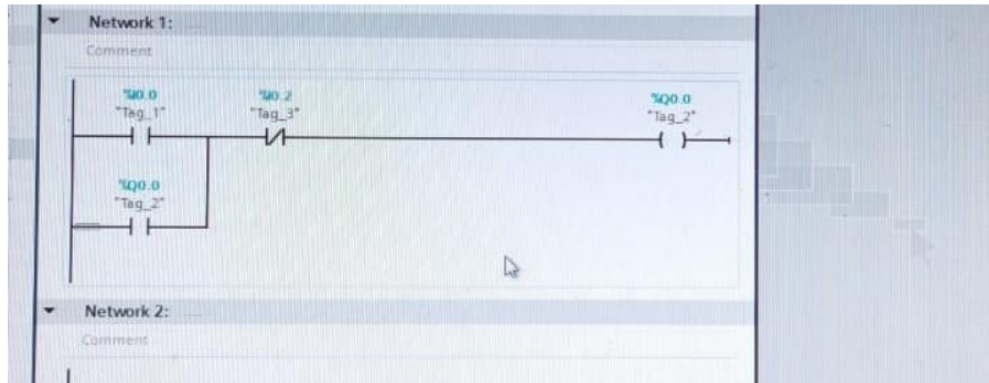


Figure 1: Ladder Diagram for Simple Boolean Operations

Additional details: Verify that the ladder logic correctly implements the Boolean expression $(S1 \text{ AND } S2) \text{ OR } (S3 \text{ AND } S4)$. Test the system by simulating input switch combinations to observe the output behavior.

4 Experimental Work

The experiment involves controlling an indicator lamp (L1, output

- The first branch connects inputs
- The second branch connects inputs

The output

Additional details: The experiment validates the correct implementation of Boolean logic in a PLC environment. Monitor the PLC's input/output status to confirm that the lamp activates only under the specified conditions.

5 Discussion

The experiment, titled "Demonstration of Simple Boolean Operations," effectively utilized a Siemens S7 1200 PLC Module or LOGO PLC, programmed through TIA Portal or LOGO Soft Comfort, to implement a ladder diagram showcasing basic Boolean logic operations. The objective was successfully met by designing a circuit that controls an indicator lamp (L1,

The ladder diagram featured two parallel branches, each embodying an AND condition: the first with inputs

The system demonstrated reliable performance, with the PLC accurately processing input conditions and controlling the output. This experiment highlights the practical utility of Boolean logic in automation, such as in control systems requiring specific input combinations to trigger outputs, like safety interlocks or sequential processes.

Potential challenges include ensuring proper switch debouncing to avoid false triggers due to electrical noise. Additionally, scaling the logic to include more inputs or complex conditions could increase programming complexity. Future experiments could incorporate additional Boolean operations, such as NOT or XOR, or explore fault detection mechanisms to enhance system robustness.